

# COMSM1302

## Overview of Computer Architecture

### Lecture 4 – Simple devices

# In this lecture

## Foundations

- Data representation, logic.

## Building blocks

- Transistors, transistor based logic, **simple devices**, storage.

## Modules

- Hex modules, memory, simple controller and processor.

## Programming

- Assembly, assembler, language, compilation phases, boot-strapping.

## Bigger systems

- ARM & Thumb, I/O, protecting shared systems, memory hierarchy, multi-processors, networks.

## Wrap-up

- More examples, historical computers, contemporary systems.

# 🔥 Today, we learn to add!

- And also...
  - Subtract
  - Select 1 signal from many
  - Distribute 1 signal to many
- The circuits shown hereafter will be drawn in [Logisim](#).
  - You can download and try yourself.
  - And you will need to in the first lab!

 


Photo by Joseph A. Carr, 1975

# The simplest of binary addition

- How to add two, single-digit binary numbers?
  - Each digit is either 0 or 1
  - There are three possible results
    - 0b00, 0b01, 0b10
    - 0, 1, 2
  - Two inputs
    - A, B
  - Two outputs
    - Sum (S), carry (C)

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# 🔥 With some Boolean Algebra


- Remember our truth tables for Boolean Algebra...
- Which operations can be used to help us generate S and C?

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1





A	B	$\neg A$	$A \wedge B$	$A \vee B$	$A \oplus B$	$A \rightarrow B$	$A \equiv B$
0	0	1	0	0	0	1	1
0	1	1	0	1	1	1	0
1	0	0	0	1	1	0	0
1	1	0	1	1	0	1	1
 
# 🔥 The half-adder

- $S = A \oplus B$
- $C = A \wedge B$
- Now let's build it with logic gates.



# 🔥 The half-adder in action

    

# Now what?

- We can add two bits together.
  - By generating a sum and a carry bit.
- How do we add multiple bits together?

**Carry example on the board**



# The full-adder




C_in	A	B	S	C_out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- $S = A \oplus B \oplus C_{in}$ 
  - **Explanation on board**
- $C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \vee B))$ 
  - **Explanation on board**
- Also valid for  $C_{out}$ 
  - $(A \wedge B) \vee (C_{in} \wedge (A \oplus B))$
  - **Why?**
 
# 🔥 The full-adder


- 8 different combinations of input
- Try them yourself!




# Now what?

- We can add two bits together.
  - By generating a sum and a carry bit.
- We can add three bits together
  - By accommodating a carry-in as well as our regular two inputs.
- How do we add multiple bits together?


# 🔥 Chaining full-adders

 

Carry chain

 

# 🔥 8-bit adder, ripple-carry adder

 

- Named **ripple-carry** because a carry signal generated at the LSB (Least Significant Bit... bit 0) of the device can affect the result on any/all more significant bits.
- Does this have any performance implications?

# Building blocks



- To recap what we've done:
  - Used Boolean Algebra as **building blocks**.
  - To build a unit capable of **adding two bits**.
    - **Half-adder**
  - Extended it to handle **carry-in**.
    - **Full-adder**
  - Chained them together to make an adder of **arbitrary size**.
    - **Ripple-carry adder**
- Now we can add anything!
  - Modern processors typically have adders between 8 and 64 bits.
  - **Why?**

# Subtraction

- Subtraction is easy if we think of it as **adding one number to a negative number**.
- So let's represent this subtraction:  
$$1 - 2 = -1$$
- As:  
$$1 + -2 = -1$$
- How to negate a number?
  - 2s complement!

# 🔥 Reminder: 2s complement



$$Y = -x_{N-1} \cdot 2^{N-1} + \sum_{i=0}^{N-2} x_i \cdot 2^i$$

-128	64	32	16	8	4	2	1	Base 10
0	0	0	0	1	0	1	0	10
1	0	0	0	1	0	1	0	-118



# 🔥 Negating in 2s complement

- Flip the bits and add one.


## Example on board

- $A - B = A + (\text{Not}(B) + 1)$
- We already have all the tools we need for this!
  - NOT gates to flip bits
  - An unused C\_in at the beginning of our adder's carry chain.


# The adder-subtractor?

- We can build an adder **or** a subtractor.
- They are **very similar**.
- Can we build one unit that does **both**?
- Almost...

# 🔥 Adder-subtractor

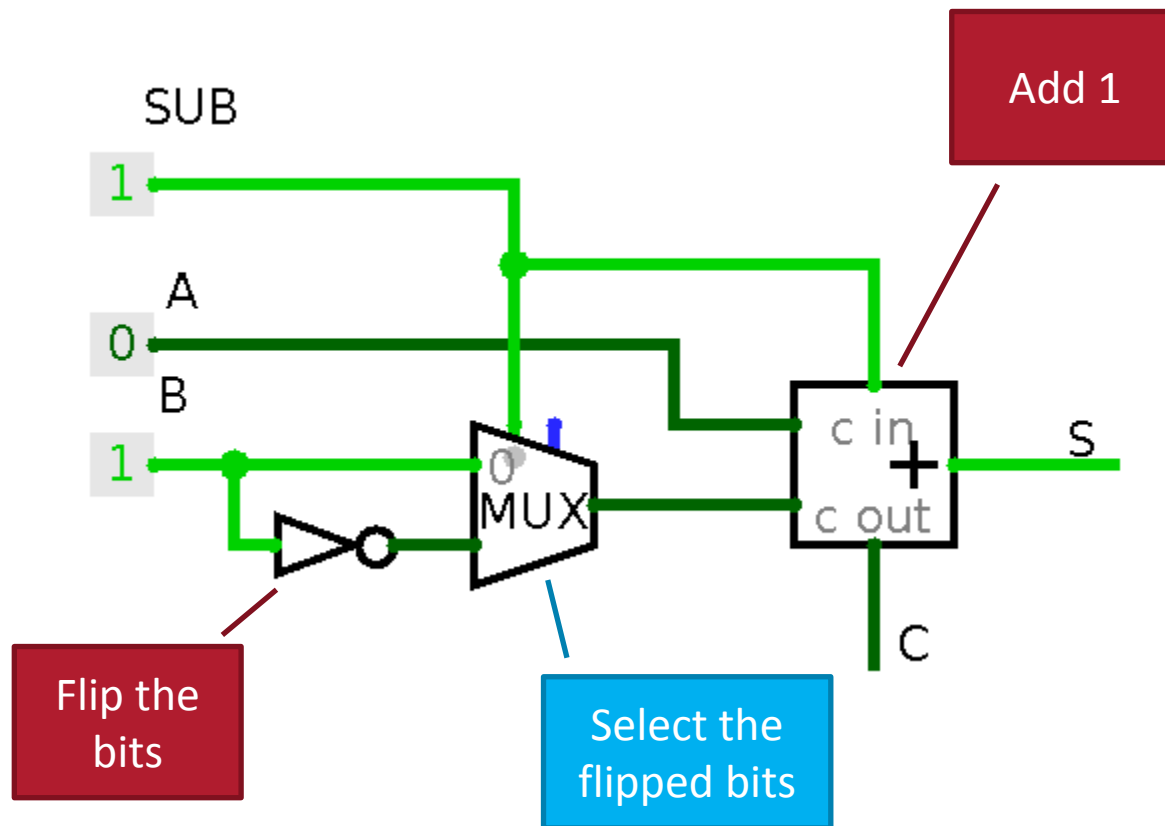

# 🔥 Choosing a signal

 

S	A	B	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


# Choosing a signal

- $(A \wedge \neg S) \vee (B \wedge S)$
- Consider  $S = 0$ 
  - $(A \wedge 1) \vee (B \wedge 0)$
  - $A \vee 0$
  - $A$
- Consider  $S = 1$ 
  - $(A \wedge 0) \vee (B \wedge 1)$
  - $0 \vee B$
  - $B$


S	A	B	Q
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1
 
# 🔥 The multiplexer


- S selects which input to propagate to the output.
- 2-to-1 multiplexer
  - 1 select bit
- **N**-to-1 multiplexers also possible
  - $\log_2(N)$  select bits needed



# 🔥 Ripple-carry adder-subtractor

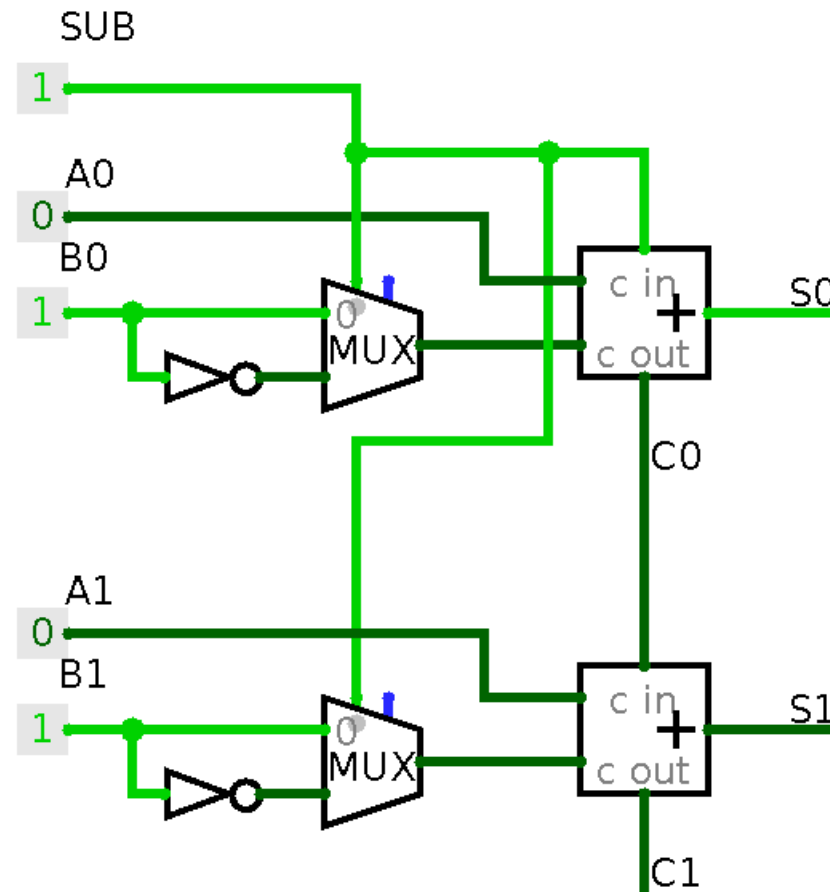

# Demultiplexer

 

- 1-to-2 demultiplexer
  - Choose **which of 2 wires** to **propagate** the input signal onto.
  - $Q0 = A \wedge \neg S$
  - $Q1 = B \wedge S$
- Instead of choosing which signal to select, we choose **where to send** a signal.
- 1-to-N demux has more logic on the select inputs.
  - That logic on its own is useful.
  - **Why?**



# Summary

- Used Boolean Algebra to build **four simple devices**:
  - Demux, Mux, Adder, Subtractor.
- Combined mux, NOT gate and adder to build **adder-subtractor**.
- We can do **basic arithmetic** with a **bunch of NAND gates**!

Imagine if we could **store** the results of that arithmetic, somehow...



# Next lecture

## Foundations

- Data representation, logic.

## Building blocks

- Transistors, transistor based logic, simple devices, **storage**.

## Modules

- Hex modules, memory, simple controller and processor.

## Programming

- Assembly, assembler, language, compilation phases, boot-strapping.

## Bigger systems

- ARM & Thumb, I/O, protecting shared systems, memory hierarchy, multi-processors, networks.

## Wrap-up

- More examples, historical computers, contemporary systems.