

# COMSM1302

## Overview of Computer Architecture

### Lecture 3 – Transistor logic, CMOS

# In this lecture

## Foundations

- Data representation, logic.

## Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

## Modules

- Hex modules, memory, simple controller and processor.

## Programming

- Assembly, assembler, language, compilation phases, boot-strapping.

## Bigger systems



- ARM & Thumb, I/O, protecting shared systems, memory hierarchy, multi-processors, networks.

## Wrap-up


- More examples, historical computers, contemporary systems.
  
# 🔥 The switch - mechanical

- Mechanical switches are very useful
  - Turn things on/off
  - With several switches, we can **encode** more useful things.
- What's wrong with them?



# 🔥 The switch - valve

 

Bank of valves from the ENIAC computer.  
Photo [source](#): TexDex, Wikimedia Commons.

- Valves or vacuum tubes.
- Current controlled by thermionic emission.
  - They have a **heating element**.
- Quicker than mechanical switches.
- Fairly reliable
  - If they're **kept on**!

# 🔥 The switch - silicon



- Silicon, the element “Si”
  - The second most **abundant element** on Earth.
- A **semiconductor**.
  - Can be constructed to pass electrons through a channel, when a voltage is applied to a **gate**.

🔥 Ore




🔥 Boule



[Source](#): Stahlkocher, Wikimedia Commons


🔥 Wafer

 

Source: James Irwin, [CC 2.0](#)

 
# 🔥 Making a switch out of silicon

- The **transistor**.
- Multiple uses
  - Amplification
  - **Switching**
- Multiple methods of construction
  - We're interested in **Integrated Circuits** (ICs), so we want **CMOS**



 
# 🔥 Modes of operation

- $A = V_{dd}$ .
- The top “switch” is **off**.
  - PMOS transistor.
- The bottom “switch” is **on**.
  - NMOS transistor
- $Q$  is “connected” to  $V_{ss}$ .



# 🔥 Modes of operation

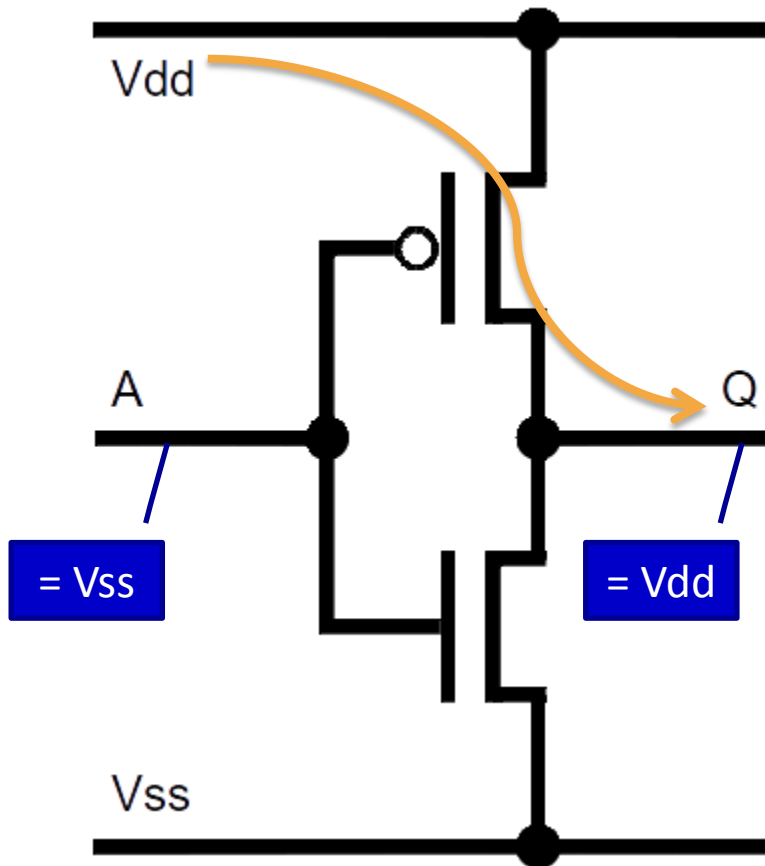


- $A = V_{ss}$ .
- The top “switch” is **on**.
- The bottom “switch” is **off**.
- Q is “connected” to Vdd.


 
# 🔥 What did we just make?



- The circuit has **four connections**.
- Two are **power supply** related.
  - Providing Vdd and Vss.
- One is an **input**.
- One is an **output**.



## 🔥 Symbolic

A	Q
Vss	Vdd
Vdd	Vss

## 🔥 Voltage

A	Q
0 V	3.3 V
3.3 V	0 V

## 🔥 Binary

A	Q
0	1
1	0

# PMOS + NMOS = CMOS



- PMOS is good for making connections to **Vdd**.
- NMOS is good for making connections to **Vss**.
- You can't make a reliable switch (or inverter) with just one type.
  - We either get 1/? or ?/0; we want 1/0.
- So we use a **pair**, one PMOS, one NMOS.
- They are **complementary**.

## CMOS


## Complementary Metal Oxide Semiconductor

# Boolean logic in CMOS


- We have a CMOS inverter.
  - Implements “not”
  - In a logic circuit, we call this a **NOT gate**.
- To build a more complex circuit, we need more than just a not gate.

**So... what can we make?**

# 🔥 NOR (NOT-OR)

 


- We could build a NOR gate.

 


**Explanation on board**

# 🔥 NAND (NOT-AND)

 

- We could also build a NAND gate.

 

**Explanation on board**

# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **NOT**  A —  — Q

## 🔥 Diagram



## 🔥 Algebra

$$\neg(A \wedge A) \equiv \neg A$$

- Idempotency axiom

## 🔥 Truth table

A	Q
0	1
1	0

# 🔥 Why NAND?



- NAND is an excellent **building block** for other Boolean logic.

- For example: **AND** 

## 🔥 Diagram


## 🔥 Algebra

## 🔥 Truth table

$$\neg(\neg(A \wedge B)) \equiv A \wedge B$$

A	B	t0	Q
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	1

- Involution axiom

 


# 🔥 Why NAND?

- NAND is an excellent **building block** for other Boolean logic.

- For example: **OR**



## 🔥 Diagram

 

## 🔥 Algebra

$$\neg(\neg(A \wedge A) \wedge \neg(B \wedge B))$$

$$\equiv \neg(\neg A \wedge \neg B)$$

$$\equiv \neg(\neg(A \vee B))$$

$$\equiv A \vee B$$



- Idempotency,  
involution & deMorgan

## 🔥 Truth table

A	B	t0	t1	Q
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1




# 🔥 Why NAND?

  


- NAND is an excellent **building block** for other boolean logic.
- NAND is **functionally complete**.
  - All gates can be expressed with NAND gates arranged in various ways.
- NOT, AND, OR as previously shown.
  - As well as **NOR**, **XOR**, **XNOR**.
 
# 🔥 Notes on NAND, NOR, inversion

- NOR is also functionally complete.
  - NOR structure is slower than NAND.
- Custom cells can be designed
  - Less silicon area, faster, ...
  - Alternative devices such as pass transistors.
    - New ways of implementing logic.
    - Can create problems with signal integrity.



# 🔥 Voltages and logic levels

 


- Simple example.
- **Ideal** inverter would be **right-angled** response.
- Steepness of position of curve dependent on transistor **properties**.
  - Size ratio between p- and n-MOS
- There is also a **delay** between a change in input producing a change in output.
 
# Summary



- Switches
  - Mechanical
  - Thermionic
  - Silicon
- Transistors
- CMOS
  - Inverter
  - NAND (functionally complete)
  - Making other gates from NAND



# In this unit

## Foundations

- Data representation, logic.

## Building blocks

- **Transistors, transistor based logic**, simple devices, storage.

## Modules

- Hex modules, memory, simple controller and processor.

## Programming

- Assembly, assembler, language, compilation phases, boot-strapping.

## Bigger systems

- ARM & Thumb, I/O, protecting shared systems, memory hierarchy, multi-processors, networks.

## Wrap-up

- More examples, historical computers, contemporary systems.